

### Oscillator Homework

1. A 555 Timer is configured for astable operation as shown in the Power Point slides. Both timing resistors (R1 and R2) are equal to  $20\text{k}\Omega$ . The timing capacitor is  $0.047\mu\text{F}$ . Find the frequency of oscillation and duty ratio of the output rectangular waveform.
2. A 555 timer is used as part of an oscillator circuit together with the coaxial capacitor from Displacement Transducer Homework problem number 3. Select a resistor value for R1 and R2 (make  $R1 = R2$ ) such that the maximum frequency is  $50\text{kHz}$  when the transducer is at one end of its travel. Then, find the resulting frequency when the transducer is at the other end of its travel. Choose the closest available resistor from the 5% tolerance values shown below.

Standard Resistor Values ( $\pm 5\%$ )						
1.0	10	100	1.0K	10K	100K	1.0M
1.1	11	110	1.1K	11K	110K	1.1M
1.2	12	120	1.2K	12K	120K	1.2M
1.3	13	130	1.3K	13K	130K	1.3M
1.5	15	150	1.5K	15K	150K	1.5M
1.6	16	160	1.6K	16K	160K	1.6M
1.8	18	180	1.8K	18K	180K	1.8M
2.0	20	200	2.0K	20K	200K	2.0M
2.2	22	220	2.2K	22K	220K	2.2M
2.4	24	240	2.4K	24K	240K	2.4M
2.7	27	270	2.7K	27K	270K	2.7M
3.0	30	300	3.0K	30K	300K	3.0M
3.3	33	330	3.3K	33K	330K	3.3M
3.6	36	360	3.6K	36K	360K	3.6M
3.9	39	390	3.9K	39K	390K	3.9M
4.3	43	430	4.3K	43K	430K	4.3M
4.7	47	470	4.7K	47K	470K	4.7M
5.1	51	510	5.1K	51K	510K	5.1M
5.6	56	560	5.6K	56K	560K	5.6M
6.2	62	620	6.2K	62K	620K	6.2M
6.8	68	680	6.8K	68K	680K	6.8M
7.5	75	750	7.5K	75K	750K	7.5M
8.2	82	820	8.2K	82K	820K	8.2M
9.1	91	910	9.1K	91K	910K	9.1M